


# MUXes

- ❖ A multiplexer is like a switchboard. You specify which input to relay to the output.
- ❖ The  $n$  selection lines determine which of  $2^n$  inputs to relay to the output.
- ❖ An enable input allows the entire MUX to be turned on or off.
- ❖ A MUX can be used to implement any Boolean function.
- ❖ In a type 0 implementation, for  $n$  variables we need  $n$  selection lines and  $2^n$  inputs. We simply apply all the variables to the selection lines and tie each input to 0 or 1 according to the desired output value. Type 0 implementations are inefficient and are rarely used.
- ❖ In a type 1 implementation, for  $n$  variables we need  $n-1$  selection lines and  $2^{n-1}$  inputs. For example, to implement a function of 3 variables, we need a  $4 \times 1$  MUX (it has 4 inputs, 2 selection lines, and of course one output). We apply  $n-1$  variables to the selection lines. Then, each input is 0, 1,  $x$ , or  $\bar{x}$  where  $x$  is the last variable.
- ❖ In a type 2 implementation, for  $n$  variables we need  $n-2$  selection lines and  $2^{n-1}$  inputs. For example, to implement a function of 4 variables, we need a  $4 \times 1$  MUX. We apply  $n-2$  variables to the selection lines. Then, each input is some simple function of the two remaining variables. External gates other than an inverter may be required for a type 2 implementation.


## MUX Example: Worksheet

$$F = \bar{B}\bar{D} + BC + ABD$$


A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

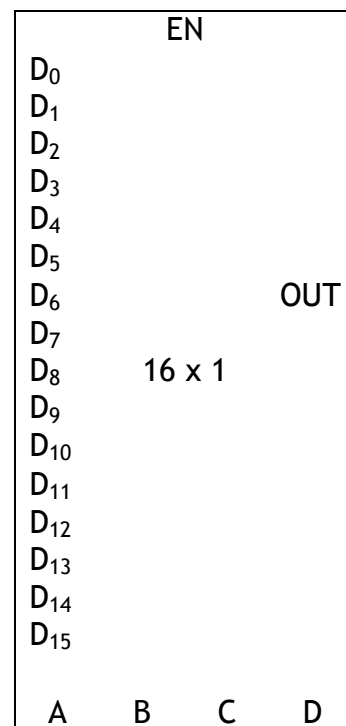

A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

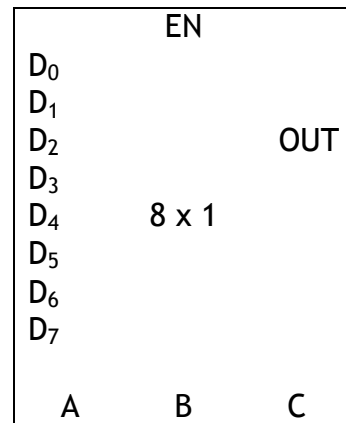

A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

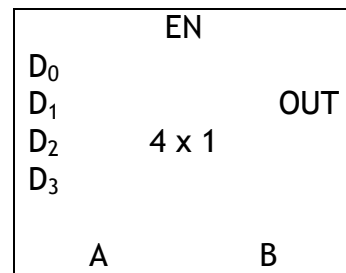

# Sequential Logic

## General

- ❖ Sequential circuits have memory. The output state depends not only on the current input states, but also on the state of the circuit itself (the current output state).
- ❖ The truth table thus contains the current output state  $Q$  as in input. The output is  $Q_{n+1}$ , representing the value of the next state of  $Q$ .
- ❖ Synchronous sequential circuits are controlled by a clock, whose pulses advance the states of each element in synchrony.

## Flip-flops

- ❖ The types of flip-flops that we will consider are: RS, D, JK, and T.
- ❖ The RS flip-flop is the basic type of flip-flop. When both inputs R and S are 0, the flip-flop retains its current state. When S is 1, it sets the flip-flop to 1. When R is 1, it resets the flip-flop to 0. When both are 1, the output is indeterminate.
- ❖ In a D flip-flop, the output is simply whatever the input is (at the time of the last clock pulse).
- ❖ A JK flip-flop is just like an RS flip-flop, except that when both J and K are 1, the flip-flop changes (toggles) between one state and the other.
- ❖ A T flip-flop toggles the output if the input is 1.
- ❖ Know the characteristic table and excitation table for each flip-flop.

## Characteristic Tables

S	R	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	ind.

J	K	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	$Q_n'$

D	$Q_{n+1}$
0	0
1	1

T	$Q_{n+1}$
0	$Q_n$
1	$Q_n'$

## Excitation Tables

$Q_n$	$Q_{n+1}$	S	R
0	0	0	d
0	1	1	0
1	0	0	1
1	1	d	0

$Q_n$	$Q_{n+1}$	J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0

$Q_n$	$Q_{n+1}$	D
0	0	0
0	1	1
1	0	0
1	1	1

$Q_n$	$Q_{n+1}$	T
0	0	0
0	1	1
1	0	1
1	1	0