

Solution Set 1

Exercises 11.8, 11.9, 11.13, 11.15, 11.17, 11.19, 11.20, 11.21, 11.22, 11.24.

11.8 (a) $(1 + 0)1 = 1 \cdot 1 = 1$
 (b) $0 + (1 \cdot 1)1 = (1 \cdot 1)1 = (1 \cdot 0)1 = 0 \cdot 1 = 0$
 (c) $(1 + 0)(1 + 1) = 1(1) = 0 \cdot 1 = 0$

11.9 (a) $F = (X + Y)\bar{X}$

X	Y	$X + Y$	\bar{X}	F
0	0	0	1	0
1	0	1	0	0
0	1	1	1	1
1	1	1	0	0

(b) $F = (Y \cdot Z)\bar{X} + X$

X	\bar{X}	Y	Z	$Y \cdot Z$	$(Y \cdot Z)\bar{X}$	F
0	1	0	0	0	0	0
0	1	0	1	0	0	0
0	1	1	0	0	0	0
0	1	1	1	1	1	1
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	0	1
1	0	1	1	1	0	1


11.13

A	B	C	A+B	A+C	(A+B)(A+C)	BC	A+BC
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

COMPARING THE LAST AND THE LAST BUT TWO COLUMNS, WE SHOWED THAT $(A+B)(A+C) = A+BC$

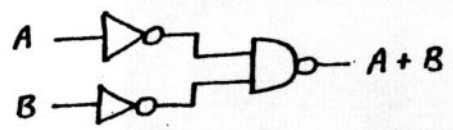11.15 BY DE MORGAN'S THM,
 $A+B \equiv \overline{\overline{A+B}} = \overline{\overline{A} \overline{B}}$


HENCE THE FOLLOWING CIRCUIT PERFORMS THE "OR" OPERATION:




11.17 FIG 11.12 SHOWS HOW TO MAKE AN XOR OUT OF TWO "NOR'S" AND ONE "AND". FROM DE MORGAN'S THM, $\overline{A+B} = \overline{A} \overline{B}$, OR, IF WE RENAME $\overline{A} = X, \overline{B} = Y$,

$$X+Y = \overline{\overline{X+Y}} \Rightarrow \overline{X+Y} = \overline{X} \overline{Y}$$


THUS A NOR GATE IS REALIZED BY

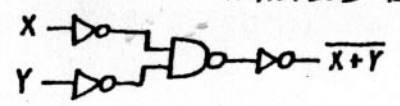

THUS FROM FIG 11.12,

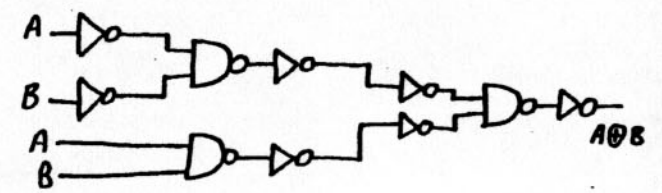

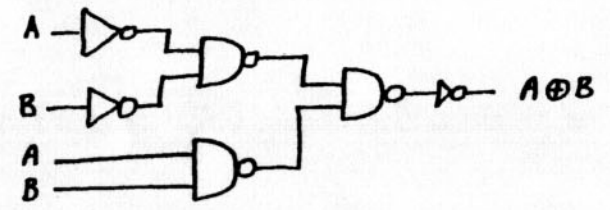(ALL INPUTS MARKED 'A' ARE CONNECTED TOGETHER, ETC.) ELIMINATING THE DOUBLE NEGATIVES, THIS SIMPLIFIES TO




THE INVERTERS CAN BE IN EITHER FORM SHOWN IN FIG. 9.33.

11.19 THE DESIRED TRUTH TABLE IS

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

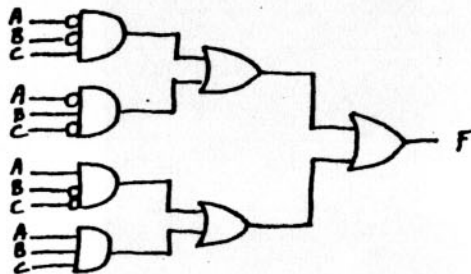
TO AVOID A 4-INPUT OR GATE WE REALIZE (USING SUM-OF-PRODUCTS METHOD) AS FOLLOWS:



11.21 THE ONLY SETS OF INPUTS FOR WHICH THE OUTPUT SHOULD BE 1 ARE


A ₁ A ₂	B ₁ B ₂
00	00
01	01
10	10
11	11

THUS WE OBTAIN FROM SUM-OF-PRODUCTS

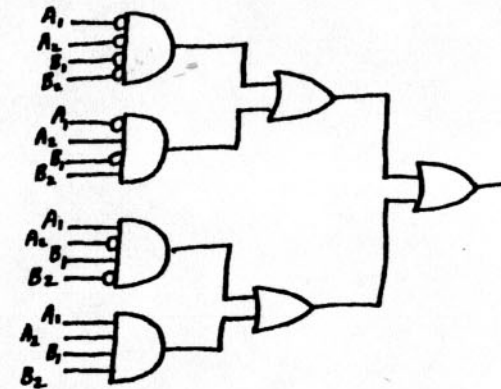


FOR THE INVERTERS USE FIG 11.33 (a or b). FOR THE OR GATES SEE PROBLEM 11.15.

11.20

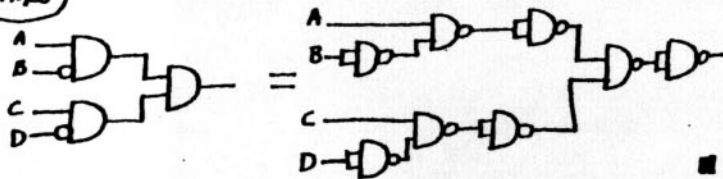


11.22

A	B	F	G	H
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

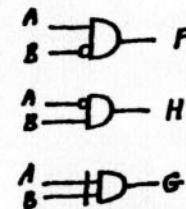

11.24

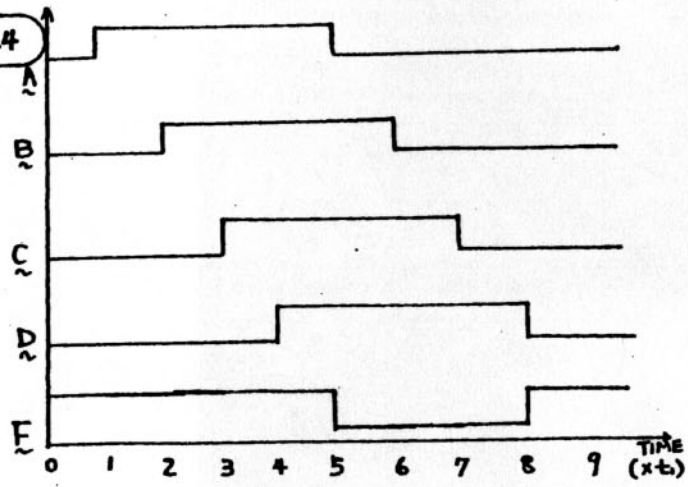

(i)

A	B	C	D	\overline{AB}	$C+D$	$F = \overline{\overline{AB}(C+D)}$
0	0	0	0	1	0	1
0	0	0	1	1	1	0
0	0	1	0	1	1	0
0	0	1	1	1	1	0
0	1	0	0	1	0	1
0	1	0	1	1	1	0
0	1	1	0	1	1	0
0	1	1	1	1	1	0
1	0	0	0	1	0	1
1	0	0	1	1	1	0
1	0	1	0	1	1	0
1	0	1	1	1	1	0
1	1	0	0	0	0	1
1	1	0	1	0	1	0
1	1	1	0	0	1	0
1	1	1	1	0	1	0