

Solution Set 5


Problems 1.13, 1.19, 2.4, 2.15, 2.23, 2.26, 2.33, 3.2, 3.3, 3.15, 3.17, 3.32

(1.13) $I = \frac{25}{6} = 4.167A = Nq$
 $= N(1.6 \times 10^{-19}) \therefore N = 2.6 \cdot 10^{19} / \text{sec}$

(1.19) $P_{\text{TOTAL}} = I(V_{12} + V_{23} + V_{34} + V_{45} + V_{56} + V_{61}) = 0$

THIS RESULT EXPRESSES ENERGY CONSERVATION. WHATEVER POWER IS DISSIPATED (IN BLOCKS WHERE VI IS POSITIVE) MUST BE BALANCED BY POWER BEING GENERATED (IN BLOCKS WHERE VI IS NEGATIVE).

(2.4)

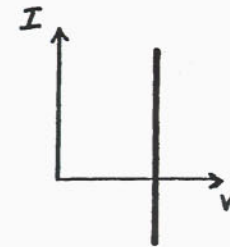

(2.15) (a) THE VOLTAGE ACROSS EACH RESISTOR IS THE SAME; CALL IT V . THEN

$$P = \frac{V^2}{R_1} + \frac{V^2}{R_2} \Rightarrow V = \left(\frac{PR_1R_2}{R_1+R_2} \right)^{1/2}$$

THE POWER DISSIPATED IN R_1 IS THEN


$$P_1 = \frac{V^2}{R_1} = P \cdot \frac{R_2}{R_1+R_2}$$

(b) LET THE CURRENT THROUGH BOTH BE I .

$$P = I^2R_1 + I^2R_2 \Rightarrow I = \left(\frac{P}{R_1+R_2} \right)^{1/2}$$

$$P_1 = I^2R_1 = P \frac{R_1}{R_1+R_2}$$

2.23 (1)

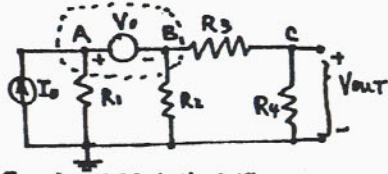

SINCE WE HAVE A VOLTAGE SOURCE AS A BRANCH, WE MERGE NODE A & B FOR THE PURPOSE OF WRITING KCL EQUATIONS.

$$V_A = V_B + V_0 \quad \text{--- (a)}$$

$$\text{KCL AT A \& B} \quad I_0 - \frac{V_A}{R_1} - \frac{V_B}{R_2} + \frac{V_C - V_B}{R_3} = 0 \quad \text{--- (b)}$$

$$\text{KCL AT C} \quad \frac{V_B - V_C}{R_3} - \frac{V_C}{R_4} = 0 \quad \text{--- (c)}$$

ONLY THREE EQUATIONS ARE NECESSARY.

(2) SOLVING THE EQUATIONS GIVES

$$V_B = \frac{R_2(R_3 + R_4)(I_0 R_1 - V_0)}{(R_1 + R_2)(R_3 + R_4) + R_1 R_2}$$

$$V_C = \frac{R_4}{R_3 + R_4} \cdot V_B$$

$$= \frac{R_2 R_4 (I_0 R_1 - V_0)}{(R_1 + R_2)(R_3 + R_4) + R_1 R_2}$$

$$V_A = V_B + V_0$$

$$= \frac{R_1 (R_3 + R_4)(V_0 + I_0 R_2) + R_1 R_2 V_0}{(R_1 + R_2)(R_3 + R_4) + R_1 R_2}$$

$$V_{OUT} = V_C$$

2.26

$$V_B - V_A = -I_1 R_1 \quad \text{--- (1)}$$

$$V_C - V_A = -I_3 R_3 \quad \text{--- (2)}$$

$$V_B - V_D = I_1 R_2 \quad \text{--- (3)}$$

$$V_C - V_D = I_3 R_4 \quad \text{--- (4)}$$

FROM (1) & (2)


$$V_B - V_C = I_3 R_3 - I_1 R_1$$

FROM (3) & (4)

$$V_B - V_C = I_1 R_2 - I_3 R_4$$

$$V_1 = 0 \Rightarrow V_B - V_C = 0$$
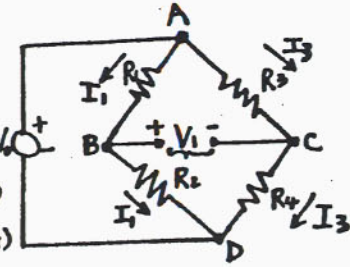
$$\Rightarrow \frac{I_3}{I_1} = \frac{R_1}{R_3} = \frac{R_2}{R_4}$$



$$\text{HENCE } R_4 = \frac{R_3}{R_1} \cdot R_2 = \frac{10K}{27K} \cdot 16K = \underline{\underline{5.9 K\Omega}}$$

2.33 THE TOTAL RESISTANCE IS THE COMPOSITE OF TEST RESISTANCE AND THE RESISTANCE OF THE VOLT METER IN PARALLEL.

$$\therefore \text{BY OHM'S LAW } I_0 = \frac{V_{AB}}{27K // 10K}$$

$$= \frac{2.16}{7.297K}$$

$$= \underline{\underline{0.296 mA}}$$

3.2) WRITE A NODE EQUATION



FOR NODE X:

$$20\text{mA} + \frac{V_B - V_A}{1000\Omega} + I = 0$$

BUT $V_A - V_B = V - 1000I$

$$\therefore 20\text{m} - \frac{V - 1000I}{1000\Omega} + I = 0$$
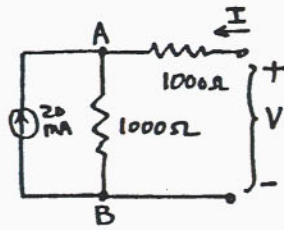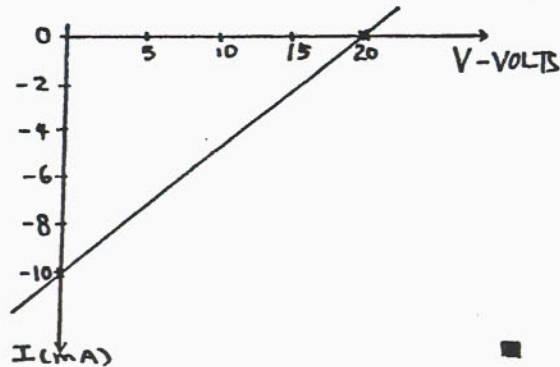
$$\Rightarrow I = 0.5 \times 10^{-3} V - 10 \times 10^{-3}$$



3.3) WRITING KCL AT THE POSITIVE TERMINAL

$$I - \frac{V}{4K} - \frac{V - 40}{4K} = 0$$

$$\Rightarrow I = \frac{V}{2000} - \frac{10}{1000}$$

THIS IS THE SAME RELATIONSHIP AS IN 3.2. SO THESE TWO SUBCIRCUITS ARE EQUIVALENT.

3.15) AN IDEAL VOLTMETER (AMMETER) IS AN

OPEN (SHORT) CIRCUIT. THUS FROM FIG 3.38,

$V_{oc} = 6V$ AND $I_{sc} = -0.19A$. IT FOLLOWS


THAT THE CORRESPONDING THÉVENIN EQUIVALENT

CIRCUIT IS CHARACTERIZED BY $V_t = V_{oc} = 6V$,

$$R_t = -\frac{V_{oc}}{I_{sc}} = -\frac{6V}{-0.19A} \approx 33\Omega \quad \text{AN}$$

I-V CHARACTERISTIC GIVEN BY BY EQ.(3-1)
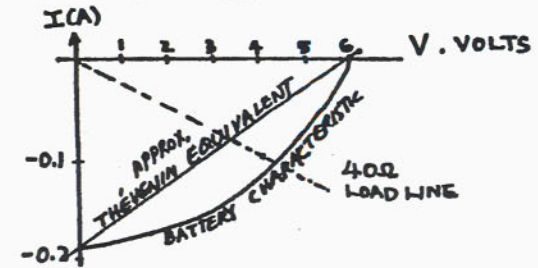
$$I = \frac{V}{R_t} - \frac{V_t}{R_t} = \frac{1}{33\Omega} V - 0.19A$$



THE TWO CHARACTERISTICS SHOWN DO NOT AGREE

BECAUSE THE BATTERY IS NON-LINEAR AND HENCE HAS

NO THÉVENIN EQUIVALENT, A THÉVENIN CIRCUIT IS

ALWAYS REPRESENTED BY A LINEAR I-V

CHARACTERISTIC.

3.17 $V_T = V_{oc} = \underline{6V}$


USING KVL

$$V = -I(40)$$

BUT $V = IR_T + V_{oc}$

$$\therefore 40 + R_T = -\frac{V_{oc}}{I} = \frac{6}{0.1125} = 53.3\Omega$$
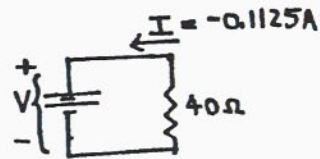
$$\Rightarrow \underline{R_T = 13.3\Omega}$$



3.32 $P_{AV} = \frac{1}{T} \int_0^T \frac{v^2(t)}{R} dt$

$$= \frac{1}{0.002} \int_0^{0.002} \frac{(0.3 \frac{t}{0.002})^2}{50} dt$$

$$= \frac{1}{0.002} \left[\frac{0.3^2}{0.002^2} t^3 / 3 (50) \right]_0^{0.002}$$

$$= \frac{1}{0.002} \left[\frac{0.3^2 (0.002)}{150} \right]$$

$$= \underline{0.6mW}$$

